

# Electronics and Microprocessing for Research, 2<sup>nd</sup> Edition



# Electronics and Microprocessing for Research, 2<sup>nd</sup> Edition:

*You Can Make It*

By

David Dubins

Cambridge  
Scholars  
Publishing



Electronics and Microprocessing for Research, 2<sup>nd</sup> Edition:  
You Can Make It

By David Dubins

This book first published 2019

Cambridge Scholars Publishing

Lady Stephenson Library, Newcastle upon Tyne, NE6 2PA, UK

British Library Cataloguing in Publication Data

A catalogue record for this book is available from the British Library

Copyright © 2019 by David Dubins

All rights for this book reserved. No part of this book may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording or otherwise, without the prior permission of the copyright owner.

ISBN (10): 1-5275-3929-6

ISBN (13): 978-1-5275-3929-7

*To Robert B. Macgregor, Jr., Gregory Man Kai Poon, Rashid Abu-Ghazalah, and to our late lab nights, past and future.*



*Epigraph by Remy Dubins*

# TABLE OF CONTENTS

List of Figures.....	xvii
List of Tables.....	xxx
Acknowledgements .....	xxxiv
Preface.....	xxxv
Section 0 .....	1
Introduction and Course Objectives	
Introduction.....	1
Why Microprocessing? .....	2
Course Objectives .....	3
Section 1 .....	5
Introduction to Electricity	
What is Electricity?.....	5
Charge.....	6
Voltage.....	7
Power .....	10
The Generalized Power Law .....	11
Resistance .....	11
Ohm's Law.....	12
Resistors .....	13
Measuring Voltage, Resistance, and Current.....	14
Using a Multimeter to Analyze Your Complicated Circuit.....	14
Measuring Overall Circuit Power Consumption and Overall Circuit Resistance .....	15
Electrical Ground .....	17
DC Ground .....	17
AC Ground .....	18
Different Ground Symbols .....	19
Types of Returns .....	19
Voltage Sources: Series vs. Parallel.....	22
Batteries in Series.....	22

Batteries in Parallel .....	22
Circuit Configurations .....	23
Kirchhoff's Voltage Law (KVL) .....	24
The Voltage Divider Equation .....	26
Kirchhoff's Current Law (KCL) .....	28
The Current Divider Equation .....	31
Calculating Current-Limiting Resistor Values for LEDs .....	33
Anode vs. Cathode: Devices with Polarity .....	34
Introduction to Switches .....	35
Breadboarding .....	37
Circuit Diagram Etiquette Example: Light Theremin .....	38
Activity 1-1: 9V Battery + LED + 10K Resistor .....	39
Activity 1-2: 9V Battery + 10K Resistor + 100K Resistor .....	41
Demo: Light Theremin .....	42
Learning Objectives for Section 1 .....	42
Section 1 - Station Content List .....	43
 Section 2 .....	44
Capacitance, Power and Logic .....	44
Capacitors .....	44
Capacitor Circuit Diagram Symbols .....	45
Capacitor Ratings .....	45
Capacitors in Series and Parallel .....	46
Capacitors: Typical Uses .....	46
Capacitor Equations .....	48
Charging a Capacitor through a Resistor .....	48
Discharging a Capacitor Through a Resistor .....	50
Voltage Divider Design: 10% Rule .....	50
Other Options for Delivering Lower Voltage .....	52
Datasheet Example: LM317 (Variable Linear Voltage Regulator) .....	53
How Hot Will My Chip Get? Heat Dissipation Calculations .....	56
Thévenin's Theorem .....	57
Thévenin's Theorem by Measurement (Using a Multimeter) .....	58
Mesh Current Method .....	61
Thévenin's Theorem Method (Theoretical) .....	64
Integrated Circuits (ICs) .....	67
PDIP/DIP .....	67
Surface Mount Technology .....	69
Logic Circuits .....	69
AND Gate: (e.g. 74HC08) .....	69
OR Gate: (e.g. 74HC32) .....	72

NOT Gate: (e.g. 74HC04) .....	73
Combining Logic Circuits .....	74
Activity 2-1: Capacitor Charging and Discharging.....	78
Activity 2-2: LM317 Voltage Regulator.....	79
Activity 2-3: Logic Gates.....	81
Learning Objectives for Section 2 .....	82
Section 2 - Station Content List .....	83
 Section 3 .....	84
Introduction to Programming in the Arduino C++ Environment	
Introduction to the Arduino Uno Microcontroller Board.....	84
Connecting a Serial LCD Module to the Arduino Uno .....	85
Your First Sketch .....	88
Basic Programming Concepts.....	89
Commenting Your Code .....	89
Storing and Accessing Data in Variables .....	91
Declaring and Using Variables .....	93
Integers.....	93
Long Integers .....	95
Global Space, Setup Function, and Loop Function .....	96
Float Variables .....	97
If...Then...Else Statements (and Logical Expressions).....	98
Bool Variables.....	101
Boolean Operators.....	102
Byte Variables.....	103
String and Char Variables .....	103
Casting Variable Types .....	105
Arrays of Variables.....	107
Char Array.....	108
Data Types: More Complicated Conversions.....	109
Defining Programming Loops in Arduino .....	111
For Loops .....	111
C++ Shorthand Increment Expressions.....	112
Do...While Loops .....	112
While Loops .....	114
For, Do...While, or While? .....	115
Omitting Curly Brackets .....	115
The Break Command .....	115
Switch Case.....	116
General Programming Tips.....	118
Activity 3-1: Programming Challenge .....	119

Learning Objectives for Section 3 .....	120
Section 3 - Station Content List .....	121
Section 4 .....	122
Arduino Pins, and Writing Functions	
Byte Variables and Digital Pins .....	122
What is a Digital Pin?.....	124
Digital OUTPUT Mode Example.....	125
Pulse Width Modulation (PWM) Example .....	126
Digital Input Mode Example .....	128
Analog Pins.....	131
Using Analog Pins as Digital Output Pins .....	132
Analog Read Example.....	132
External Analog Reference: AREF Pin.....	134
Arduino Pin Conflicts .....	135
Arduino Digital and Analog Pins: Summary Tables.....	136
The Serial Monitor.....	137
The Serial Plotter .....	138
Subroutines and Functions .....	138
Properties of Functions.....	139
Void Functions .....	139
Call-by-Value vs. Call-by-Reference .....	141
Float Functions.....	142
Integer (and other) Functions .....	144
Function DOs and DON'Ts.....	144
#define and #ifdef Statements .....	145
General Programming Etiquette .....	147
Activity 4-1: NTC Thermistor Circuit .....	148
Calibrating a Thermistor .....	149
Two-Term Exponential Thermistor Equation .....	149
Learning Objectives for Section 4 .....	153
Section 4 - Station Content List .....	154
Section 5 .....	155
Switching Higher Power Devices: Relays, Transistors, TRIACs	
Voltage and Current Limitations of the Arduino Uno .....	155
Relays .....	157
High Side Switching vs. Low Side Switching.....	160
Powering a Relay with a Separate Supply.....	161
Vin Pin: Arduino Uno .....	161
Diodes (P-N Junction, or Rectifier Diodes) .....	162

Transistors.....	165
Bipolar Junction Transistors (BJTs).....	165
NPN Transistors: Selecting a Base Resistor Value .....	167
NPN Transistors in the Active Region .....	170
Darlington Pairs .....	172
Current Gated vs. Voltage Gated .....	173
MOSFETs .....	174
TRIACs.....	177
BT139-600E (TRIAC) .....	180
Protecting your Circuit from DC Motors .....	180
Protection Diode.....	180
Reducing DC Motor Noise with Capacitors.....	181
Activity 5-1: Hot Plate Thermostat .....	182
Activity 5-2: Transistor as a Switch for a DC Motor .....	184
Parsing Serial Data.....	187
Activity 5-3: MOSFET as a Switch for a DC Motor .....	187
Learning Objectives for Section 5 .....	188
Section 5 - Station Content List .....	190
Section 6 .....	191
Process Control	
When “Close Enough” Isn’t Close Enough .....	191
How a DC Motor Works .....	192
Using an H-Bridge to Control Motor Speed and Direction.....	192
L298N H-Bridge Motor Driver Module.....	194
Stepper Motors.....	197
28BYJ-48 Stepper Motor with ULN2003 Motor Driver .....	198
Nema-17 Stepper Motor with A4988 Motor Driver.....	200
Servo Motors.....	205
System Control Strategies.....	206
Open-Loop Control.....	206
Feed Forward Control .....	208
Feedback Control .....	211
On-Off Controller.....	212
Proportional (P) Controller.....	213
Proportional-Integral (PI) Controller.....	217
Proportional-Integral-Derivative (PID) Controller.....	219
Combining Feedback Strategies .....	222
Activity 6-1: L298N Motor Driver Controlling a DC Motor .....	224
Activity 6-2(a): 28BYJ-48 Stepper Motor .....	225
Activity 6-2(b): Nema-17 Stepper Motor .....	226

Activity 6-3: SG90 Servo Control .....	228
Activity 6-4: PID Control of a 12V CPU Fan.....	230
Learning Objectives for Section 6 .....	231
Section 6 - Station Content List, Activities 6-1 & 6-3 .....	233
Section 6 - Station Content List, Activities 6-2(a,b), 6-4.....	234
 Section 7 .....	235
<b>Operational Amplifiers</b>	
Introduction.....	235
Open Loop Configuration (Comparator) .....	236
Closed Loop Configuration.....	237
Buffer .....	237
Op-Amp Characteristics.....	239
Output Short-Circuit Current.....	239
Gain in dB (decibels).....	239
Headroom .....	239
Slew Rate .....	242
Unity Gain Bandwidth .....	243
Inverting Amplifier .....	243
Biasing the Output of an Inverting Amplifier .....	246
Non-Inverting Amplifier .....	247
Biasing the Output of a Non-Inverting Amplifier .....	249
Differential Amplifier .....	250
Summing Amplifier (Inverting) .....	251
Summing Amplifier (Non-Inverting).....	252
Summing Amplifier (Non-Inverting) Equations Solved .....	253
Negative Voltage?.....	260
Solution 1: Using a Virtual Ground.....	260
Solution 2: Negative Voltage Generator .....	261
Solution 3: Negative Supply Line from an ATX Power Supply ..	262
Op-Amps Can Do Calculus .....	262
Signal Attenuation: Reducing the Voltage.....	263
Activity 7-1: Load Cell Scale .....	263
Activity 7-2: pH Meter.....	267
Learning Objectives for Section 7 .....	271
Section 7 - Station Content List, Activity 7-1 .....	272
Section 7 - Station Content List, Activity 7-2.....	273
 Section 8 .....	274
<b>Data Filtering, Smoothing, and Logging</b>	
Data Filtering .....	274

Low-Pass Filters (LPFs).....	275
High-Pass Filters (HPFs).....	280
Inverting AC Amplifier.....	281
Blocking the DC in your Signal: Charge Coupling.....	283
Higher Order Filters.....	284
Band-Pass Filters.....	284
Second Order Low-Pass and High-Pass Filters.....	286
Operational Amplifiers: Practical Considerations.....	287
Impedance Considerations: Op-Amp Inputs .....	288
Impedance Considerations: Op-Amp Output .....	288
Measuring Output Impedance .....	290
Measuring Input Impedance.....	290
Practical Strategies to Reduce Signal Noise .....	291
Measuring Noise.....	294
Data Smoothing .....	295
Mean Filter .....	295
Median Filter .....	296
Mode Filter .....	297
Mean Filter with Threshold Rejection.....	298
Data Logging .....	300
Arduino TimeLib.h Library .....	301
Using millis() Instead of delay() .....	302
Logging through the Serial Port.....	304
Logging to an External microSD Card .....	305
Logic Shifters .....	305
Activity 8-1: Noise Reduction .....	307
Activity 8-2: Data Smoothing .....	307
Activity 8-3: Data Logging to an SD Card .....	309
Learning Objectives for Section 8 .....	311
Section 8 - Station Content List .....	312
Section 9 .....	313
Design Project Guidance	
Introduction.....	313
Design Project Selection .....	313
Design Project Assessment .....	313
What if my design project doesn't work?.....	317
Code Snippets and Examples .....	318
Serial Monitor Menu .....	318
Using EEPROM: Memory that Doesn't Forget! .....	320
Generating Beeps to Alert your User: Arduino Tone Library .....	323

Programming One Button with Multiple Functions .....	324
Measuring Light Intensity .....	325
Photoresistors .....	325
Photodiodes .....	328
Phototransistors .....	329
Integrated Packages .....	330
Measuring Time Duration with Interrupts .....	336
Op-Amp Comparator with Bias Voltage: Turning an Analog Signal into a HIGH or LOW Digital Level .....	337
Matrix Keypads and LED Matrix Displays .....	338
Charlieplexing LEDs .....	341
Need More Digital Pins? .....	343
Shift-Out Registers .....	343
Shift-In Registers .....	345
Bareduino – Running the ATmega328 Alone .....	348
Learning Objectives for Section 9 .....	351
 Section 10 .....	352
Advanced Topics in Programming	
Controlling MCU Registers, Interrupts and Timers .....	352
Bitwise Operations .....	352
Bitwise AND (&) .....	353
Bitwise OR ( ) .....	354
Bitwise NOT (~) .....	355
Bitwise XOR (^) .....	356
Shifting Bits with “<<” and “>>” .....	357
Bitwise Operators: Short Forms .....	358
Introduction to Port Manipulation .....	360
Worked Example: Fast Analog Read .....	361
Fast Digital Read and Write .....	365
Interrupts .....	368
Internal (Pin Change) Interrupts .....	370
Never Miss a Button Push Again .....	371
Rules for Writing an Interrupt Service Routine .....	372
Customized Frequencies for PWM .....	373
Timer 0 .....	374
Timer 1 .....	377
Timer 2 .....	379
Timing your Interrupt Service Routines with CTC Mode .....	382
Sleep Mode .....	386
Wake on Pin Change .....	386

Wake on Timeout of Watchdog Timer.....	387
Resetting the MCU .....	389
Reset with a Watchdog Timer .....	389
Hard Wiring a Digital Pin to the RESET Pin .....	390
Advanced Formating and Variable Type Conversions .....	391
Secrets of Serial.print() .....	391
Additional String Conversion Commands.....	394
Comparing Strings.....	394
Arrays of Strings and Arrays of Char Arrays .....	395
Using Special Characters .....	396
Char Arrays: Advanced Functions .....	397
Structures .....	399
Unions.....	402
Increment Operators as Array Index Values.....	403
 Appendix .....	405
Troubleshooting Guide .....	405
Troubleshooting Flowchart .....	409
Troubleshooting Zones.....	409
UTF-8 and ASCII Tables .....	410
Tips to Optimize Sketch Memory .....	414
Using a 555 Timer as an External Clock .....	420
Common Fixed Resistor and Capacitor Values .....	422
.ino Files .....	423
triacDimmer.ino (Section 5).....	423
Thermostat.ino (Section 5).....	423
4WStepper.ino: 4-Wire Stepper Control (Section 6).....	425
4WStepper_noLib: 4-Wire Stepper Control (no library required).....	425
PID.ino (Section 6).....	427
QuickStats.h (Section 8).....	429
TimedISR_N.ino (Section 10)	432
Derivation for $\bar{V}_{in(+)}$ (Section 7) .....	433
Arduino Uno Pin-out Diagram.....	436
ATmega328 Pin-out Diagram .....	437
ATtiny85 Pin-out Diagram .....	437
Ohm's Law Equation Table .....	437
List of Circuit Diagram Symbols .....	438
Variable Type Conversion Chart .....	439
List of Abbreviations .....	440

Bibliography .....	442
Index .....	451

## LIST OF FIGURES

Figure 1-1. Mobile valence electron in the outer shell of a copper atom.....	5
Figure 1-2. Different ways of illustrating wire connections on a circuit diagram. ....	6
Figure 1-3. A battery provides a constant voltage source.....	7
Figure 1-4. Conventional current vs. actual flow of electrons.....	8
Figure 1-5. Cathode and anode reactions of an alkaline battery. (Besenhard 1999).....	8
Figure 1-6. Circuit symbols and voltage vs. time diagrams for Direct Current (DC) and Alternating Current (AC) voltage sources. ....	10
Figure 1-7. Using DC batteries in series.....	10
Figure 1-8. Resistance is the proportional current of electrons induced by a difference in voltage. For an ohmic device like a fixed-value resistor, this relationship is linear. ....	12
Figure 1-9. Circuit diagram symbols for fixed-value resistors. ....	13
Figure 1-10. Measuring voltage (left), resistance (middle), and current (right) using a digital multimeter. ....	14
Figure 1-11. Measuring the overall voltage, current, and power consumption of your circuit. ....	15
Figure 1-12. Circular and linear methods of drawing the same circuit.....	18
Figure 1-13. AC household power outlet (North America). AC cable wire colours are indicated for North America and the United Kingdom. ....	18
Figure 1-14. Common symbols for earth ground (left), chassis ground (middle), and floating ground (right).....	19
Figure 1-15. Floating return, drawn as it would be wired (left), using circular circuit diagram format (middle), and linear circuit format (right).....	20
Figure 1-16. Chassis return. Note that optionally, the chassis can also be connected to earth ground, to reduce shock hazard in case of an accidental short circuit. ....	21
Figure 1-17. Earth return. Even though most battery-powered devices are floating, circuit diagrams tend to use the earth ground symbol for them regardless.....	21
Figure 1-18. Voltage is additive, and total current capacity remains constant when batteries are wired in series. ....	22

Figure 1-19. Current capacity is additive, and voltage remains constant when batteries are wired in parallel. ....	23
Figure 1-20. Three ways of connecting electronic components: basic, in series, and in parallel. ....	23
Figure 1-21. Kirchoff's Voltage Law applied to resistors in series. ....	24
Figure 1-22. Derivation of the voltage divider equation. ....	25
Figure 1-23. The voltage divider equation. The voltage across each resistor is proportional to the ratio of its contribution to the total resistance, $R_1+R_2$ .....	26
Figure 1-24. Worked example for the voltage divider equation. ....	27
Figure 1-25. Kirchoff's Current Law example. ....	28
Figure 1-26. KCL applied to resistors in parallel. Note that the drawing on the left is equivalent to the drawing on the right electrically. Resistors in parallel can be represented either way. ....	28
Figure 1-27. KCL for two resistors in parallel.....	30
Figure 1-28. The current divider equation, for two resistors in parallel. ....	31
Figure 1-29. Worked example for the current divider equation. ....	32
Figure 1-30. Calculating the resistance of a current-limiting resistor for an LED. The LED symbol is labelled $D_1$ (for diode 1) in the circuit diagram. ....	33
Figure 1-31. LED & resistor circuit, with anodes and cathodes labeled....	34
Figure 1-32. Circuit diagram symbol (left) and example (right) of a latching on/off switch. ....	35
Figure 1-33. Momentary switch connections. ....	36
Figure 1-34. Breadboard layout (top). Transparent arrows show how the power rails are connected by row, and middle pins are connected by column. The adhesive backing was peeled from the underside of a breadboard, revealing directionality of the internal rails (bottom).....	37
Figure 1-35. Light theremin circuit diagram. If a legend is used, values next to the circuit diagram symbols may be omitted. ....	38
Figure 1-36. Schematic for Activity 1-1. Note: the <i>longer</i> wire on the LED is the positive side (anode). ....	39
Figure 1-37. Schematic for Activity 1-2. ....	41
Figure 1-38. Section 1 station setup. ....	43
Figure 2-1. Electron build-up and flow upon capacitor charging and discharging. ....	45
Figure 2-2. Circuit symbols for different types of capacitors. ....	45
Figure 2-3. Electrolytic (left) and ceramic (right) capacitors. ....	46
Figure 2-4. Calculating total capacitance of capacitors in parallel and in series. ....	46

Figure 2-5. A charge-discharge circuit. Holding down SW <sub>1</sub> charges the capacitor. Once charged, holding down SW <sub>2</sub> discharges the capacitor .....	47
Figure 2-6. Capacitors can remove high frequencies from a signal (e.g. in an RC low-pass filter), low frequencies (e.g. in a CR high-pass filter), rectify an AC signal to DC, and reduce fluctuations in a noisy power supply.....	47
Figure 2-7. A circuit to illustrate charging and discharging a capacitor through a resistor.....	48
Figure 2-8. It takes about three time constants ( $3 \times \tau$ ) for a capacitor to charge through a resistor.....	49
Figure 2-9. It takes about three time constants ( $3 \times \tau$ ) for a capacitor to discharge through a resistor .....	50
Figure 2-10. Solving for R <sub>2</sub> using the voltage divider equation. ....	50
Figure 2-11. Calculating the value of the bleed resistor, using the 10% Rule. ....	51
Figure 2-12. Solved circuit using the 10% Rule. ....	52
Figure 2-13. Split supply. ....	53
Figure 2-14. LM317 pin-out diagram (left) and pin assignments (right)...	54
Figure 2-15. LM317 used as an adjustable regulator circuit with improved ripple rejection. (Texas Instruments Inc 2016a) .....	55
Figure 2-16. LM317 used as a current limiter. (Texas Instruments Inc 2016a).....	56
Figure 2-17. Circuit diagram symbol for a 10 mA current source.....	56
Figure 2-18. Heat sink for TO-220 package. The silicon layer and plastic nut keep the body of the package insulated from the heat sink, to reduce the chances of a short circuit. ....	56
Figure 2-19. Thévenin's Theorem in a nutshell. Any complicated network of resistors, capacitors, and sources from the perspective of a single component (at connections a and b) may be represented as a voltage source in series with a resistor.....	58
Figure 2-20. Example circuit for Thévenin's Theorem. First step: identify two terminals of interest, and label them <b>a</b> and <b>b</b> .....	59
Figure 2-21. Remove the load from the example, and measure V <sub>ab</sub> . ....	59
Figure 2-22. Measure i <sub>sc</sub> across terminals a and b. ....	59
Figure 2-23. Thévenin Equivalent Circuit .....	60
Figure 2-24. Thévenin Equivalent Circuit with load replaced.....	60
Figure 2-25. Short all voltage sources, remove all current sources, then measure R <sub>TH</sub> .....	61
Figure 2-26. Norton Equivalent Circuit.....	61
Figure 2-27. Example for the Mesh Current Method. ....	62

Figure 2-28. Number each inside loop, draw current arrows, and label each junction.....	62
Figure 2-29. Perform KCL on junction A.....	63
Figure 2-30. Perform KCL on junction B.....	63
Figure 2-31. Identify points a and b around the load.....	65
Figure 2-32. Remove the load, then calculate the voltage difference between points a and b.....	65
Figure 2-33. Circuit diagrams can be deceptive. These four circuits all depict two resistors in parallel, from points <b>a</b> to <b>b</b> .....	66
Figure 2-34. Thévenin Equivalent circuit, with load replaced.....	67
Figure 2-35. DIP chips are great for prototyping with breadboards. ....	67
Figure 2-36. Pin numbering for DIP chips runs counterclockwise, starting from the bottom left pin.....	68
Figure 2-37. Logic symbol for an AND gate.....	69
Figure 2-38. Pinout diagram for the 74HC08 AND chip.....	70
Figure 2-39. Circuit diagram to test out the functionality of an AND gate. Pull-down resistors protect against floating pin states when the DIP switches are open. ....	70
Figure 2-40. Venn diagram for a 2-input AND gate.....	71
Figure 2-41. Logic symbol for a 2-input OR gate (top). Pinout diagram for the 74HC32 OR chip (bottom). ....	72
Figure 2-42. Circuit diagram to test out the functionality of an OR gate. .	72
Figure 2-43. Venn diagram for a 2-input OR gate .....	73
Figure 2-44. Logic symbol for a NOT gate (top). Pinout diagram for the 74HC04 NOT chip (bottom). ....	73
Figure 2-45. Schematic to test out the functionality of a NOT gate. ....	73
Figure 2-46. Venn diagram for a NOT gate.....	74
Figure 2-47. An AND gate combined with a NOT gate is equivalent to a NAND gate. ....	74
Figure 2-48. Venn diagram for a 2-input NAND gate.....	74
Figure 2-49. An OR gate combined with a NOT gate is equivalent to a NOR gate. ....	75
Figure 2-50. Venn diagram for a 2-input NOR gate. ....	75
Figure 2-51. XOR gate, meaning “exclusive OR”.....	75
Figure 2-52. Venn diagram for a 2-input XOR gate. ....	76
Figure 2-53. XNOR gate, meaning “NOT exclusive OR”, or “exclusive NOR”. ....	76
Figure 2-54. Venn diagram for a 2-input XNOR gate. ....	76
Figure 2-55. Symbolic logical representation of Example 1(a). ....	77
Figure 2-56. Venn diagram for Example 1(a).....	77
Figure 2-57. Symbolic logical representation of Example 2(a). ....	77

Figure 2-58. Venn diagram for Example 2(a).....	77
Figure 2-59. Circuit diagram for Activity 2-1. ....	78
Figure 2-60. Schematic for Activity 2-2. Note: Pin 3 of the 1K trim is not connected. ....	80
Figure 2-61. Circuit diagram for Activity 2-3 (from Figures 2-38 and 2-39). ....	81
Figure 2-62. Section 2 station setup. ....	83
Figure 3-1. Arduino Uno R3 board layout (DIP version). ....	85
Figure 3-2. Connecting the MCU to a serial LCD module. ....	86
Figure 3-3. Arduino Uno (SOIC version) connected to serial LCD module and laptop. ....	86
Figure 3-4. Arduino IDE sketch window. ....	87
Figure 3-5. Our first Arduino Uno sketch, with section and line comments. ....	91
Figure 4-1. Digital and analog pins of the Arduino Uno MCU. ....	123
Figure 4-2. Schematic to connect an LED to the Uno's digital pin 6, using a breadboard. ....	125
Figure 4-3. Circuit diagram for schematic in Figure 4-2. ....	126
Figure 4-4. Pulse width modulation (PWM), illustrated with different duty cycles. ....	127
Figure 4-5. Gaining and shifting the sin() function to the working PWM range [0-255]. ....	128
Figure 4-6. LED circuit (left) and momentary switch circuit (right). ....	130
Figure 4-7. LM35 temperature sensor. (Texas Instruments Inc. 2017) ...	132
Figure 4-8. A potentiometer can be set up as a variable resistor (rheostat), or a voltage divider. The wiper (middle pin) sweeps across a length of resistive material. ....	133
Figure 4-9. LED circuit (left) and potentiometer set up as a voltage divider (right). ....	133
Figure 4-10. The AREF pin lets you set the voltage of the highest div (1023). Range: 0-5V. ....	134
Figure 4-11. Thermistor + LED circuit. Resistor R <sub>1</sub> is the sense resistor. ....	151
Figure 4-12. Section 4 station setup. ....	154
Figure 5-1. A high voltage induces a magnetic field, pulling a switch closed. ....	156
Figure 5-2. Relay circuit diagram symbol (Single Pole, Double Throw - SPDT). ....	157
Figure 5-3. Two common types of relays: DPST and DPDT. ....	158
Figure 5-4. Internal circuit diagram of a SPDT relay module. An opto-coupler isolates the Arduino Uno from the relay supply.	

Some relay modules allow for a separate ground for the supply powering the relay, although in the lab we will power the relay module using the Arduino +5V pin. (ELECFREAKS wiki 2015).....	158
Figure 5-5. Using a SPDT relay as a normally open (NO) switch vs. a normally closed (NC) switch. The switch terminals have been sketched into the relay module boxes to help illustrate switching direction.....	159
Figure 5-6. The relay module on the left is wired as a high side switch (above the load). The relay module on the right is wired as a low-side switch (below the load) .....	160
Figure 5-7. The relay module on the left is powered using the Arduino Uno, which can introduce a lot of switching noise to your measurements. The relay module on the right is powered using a separate +5V DC adapter.....	161
Figure 5-8. The Vin pin gives you access to the power supply voltage used to power the Uno, before the on-board 5V voltage regulator. ....	162
Figure 5-9. Diode symbols: LED (left), and general diode symbol (right). .....	162
Figure 5-10. Anatomy of a diode. Silicon has 4 outer valence electrons. When doped with boron (3 outer valence electrons), a space is formed capable of temporarily accepting an electron (left). When doped with phosphorus (5 outer valence electrons), there is an extra electron, capable of flowing (right). .....	163
Figure 5-11. When conventional current tries to flow from anode to cathode, a diode is forward biased, and electrons can jump across the P-N junction.....	163
Figure 5-12. When conventional current flows from cathode to anode, a diode is said to be reverse biased, and electrons can no longer cross the P-N junction.....	164
Figure 5-13. 1N4007 diode. A stripe indicates the brick wall (location of N-terminal). .....	164
Figure 5-14. Circuit to illustrate how a transistor works. Q <sub>1</sub> is a 2N2222 NPN transistor in a TO-92 package. (ON Semiconductor Corp 2013).....	165
Figure 5-15. Worked example for the 10% Current Rule.....	168
Figure 5-16. An NPN transistor configured as a common emitter amplifier. .....	170
Figure 5-17. Calculating the voltage changes around the three terminals of a bipolar junction transistor used as a common emitter amplifier in Figure 5-16.....	171
Figure 5-18. A Darlington pair of NPN transistors.....	172
Figure 5-19. A regular LED as a light sensor.....	173

Figure 5-20. When $V_{GS(th)}$ is applied to the gate terminal, an N-channel MOSFET allows conventional current to flow from drain to source.	175
Figure 5-21. Pin-out diagram for 2N7000 N-channel MOSFET.	176
Figure 5-22. Circuit diagram symbol for a TRIAC.	177
Figure 5-23. A TRIAC, controlled by microcontroller digital pin for a resistive load connected to 60 Hz, 120V AC power. This circuit can interrupt the hot wire in the middle of an extension cord, to create a high-side switch.....	177
Figure 5-24. TRIAC with zero-crossing detector, for an inductive or resistive load. This circuit is a low-side AC dimming switch. ....	179
Figure 5-25. Forward phase dimming (left) and reverse phase dimming (right) with a TRIAC. The TRIAC is switched on and off strategically to chop an AC supply into narrower widths to dim a resistive load. (Coleman 2015)	179
Figure 5-26. Protection diode on a DC motor. In this configuration, the DC motor can only spin in one direction.	181
Figure 5-27. Noise-reducing capacitor on “Bob”, the laboratory video rover. These capacitors fixed his nasty resetting problem.	182
Figure 5-28. Circuit diagram for Activity 5-1: hot plate thermostat.....	183
Figure 5-29. Schematic for Activity 5-2: NPN transistor-controlled DC motor.	185
Figure 5-30. Floppy drive connector of an ATX power supply, capable of supplying up to 3 amps. ATX power supplies are salvageable from old desktop computers.	185
Figure 5-31. Circuit diagram for Activity 5-3: MOSFET-controlled DC motor.	188
Figure 5-32. Section 5 station setup.	190
Figure 6-1. The rotor coil of a motor (left) will spin according to Fleming’s left hand rule (right).....	192
Figure 6-2. Simple H-Bridge configuration.....	193
Figure 6-3. Protection diodes for an H-bridge.	194
Figure 6-4. L298N H-bridge module. This module comes with an on-board regulator that you can also use to power the logic side of your circuit. Check the top and underside of the module to confirm pin and screw terminal identities, as some modules may vary.....	195
Figure 6-5. Pin jumpers in the <i>open</i> position (top), and in the <i>closed</i> position (bottom), L298N module.	196
Figure 6-6. A Nema-17 bipolar stepper motor with 5mm shaft coupler..	197
Figure 6-7. Circuit diagram symbols for unipolar (left) and bipolar (right) stepper motors. A unipolar stepper motor can be controlled by 4	

switches, whereas a bipolar stepper motor requires two H-bridges to operate.....	198
Figure 6-8. A 28BYJ-48 stepper motor, with ULN2003 driver module..	198
Figure 6-9. Connecting a Nema-17 to a microprocessor with an A4988 stepper motor driver. Build this circuit with the power off.....	201
Figure 6-10. A4988 motor driver. White arrow points to trim potentiometer.....	202
Figure 6-11. MG995 servo with shaft attachments.....	205
Figure 6-12. Functional block diagram of toaster control system. ....	207
Figure 6-13. Toaster setting dial – an example of open-loop feedback control.....	208
Figure 6-14. Adding a sensor to a system on an INPUT stream and using that information to adjust DRIVE is a feed-forward strategy...	209
Figure 6-15. Example of a feed forward control system. ....	210
Figure 6-16. Example of a feedback control system.....	211
Figure 6-17. Example of a proportional feedback control system. ....	213
Figure 6-18. Undamped feedback response.....	214
Figure 6-19. Over-damped feedback response. ....	215
Figure 6-20. Under-damped feedback response, illustrating the concepts of rise time, overshoot, and settling time. ....	216
Figure 6-21. Finding a critically-damped feedback response. ....	217
Figure 6-22. Over-damped feedback response illustrating the effects of an integral gain. This response overshoots a little, because of integral wind-up.....	218
Figure 6-23. Adjusting the derivative gain to attain the setpoint.....	221
Figure 6-24. A simple PID control algorithm.....	222
Figure 6-25. Circuit diagram for Activity 6-1. ....	224
Figure 6-26. Circuit diagram for Activity 6-2(a): 28BYJ-48 stepper motor with ULN2003. ....	225
Figure 6-27. Circuit diagram for Activity 6-2(b): Nema-17 stepper motor with A4988. ....	227
Figure 6-28. Circuit diagram for Activity 6-3. ....	229
Figure 6-29. Circuit diagram for Activity 6-4. ....	230
Figure 6-30. Functional block diagram for Activity 6-4.....	231
Figure 6-31. Station setup for Activities 6-1 and 6-3. Not shown: ATX power supply.....	233
Figure 6-32. Station setup for Activities 6-2 and 6-4. Not shown: ATX power supply.....	234
Figure 7-1. Circuit diagram symbol for an operational amplifier. ....	236
Figure 7-2. Open-loop configuration of an operational amplifier. ....	236
Figure 7-3. Buffer (or voltage follower) configuration of an op-amp. ....	237

Figure 7-4. The voltage output of an ideal buffer follows the voltage input ( $V_{out}=V_{in}$ ) .....	238
Figure 7-5. Maximum peak output voltage vs. frequency for the TL07x op-amp series ( $R_L=2k\Omega$ , $T=25^\circ C$ ). (Texas Instruments Inc 2017)....	240
Figure 7-6. The op-amp on the right can swing higher because larger voltages are provided to the power rails. ....	240
Figure 7-7. Op-amp headroom means that the output of the op-amp can't swing all the way to the power rails. This is an illustration of the TL07x series, when the op-amp is supplied with $\pm 5V$ .....	241
Figure 7-8. The output of a typical op-amp will not be able to swing all the way to ground, if the negative rail is connected to ground.....	241
Figure 7-9. A rail-to-rail op-amp is able to swing its output within microvolts of the power rails (virtually no headroom).....	242
Figure 7-10. Inverting amplifier configuration of an op-amp.....	243
Figure 7-11. An op-amp's $V_{out}$ is constrained by the voltage connected to its power rails.....	244
Figure 7-12. Input and output of an inverting amplifier (gain of -2). ....	245
Figure 7-13. Configuration (left) and performance (right) of an inverting amplifier (unity gain).....	245
Figure 7-14. Biasing an inverting amplifier.....	246
Figure 7-15. Using a voltage divider to generate a bias voltage for an inverting amplifier .....	247
Figure 7-16. Configuration (left) and example performance (right) of a non-inverting amplifier .....	248
Figure 7-17. Calculating $V_{out}$ for a non-inverting amplifier. ....	248
Figure 7-18. Configuration (left) and example performance (right) of a non-inverting operational amplifier, with a bias voltage. ....	249
Figure 7-19. Differential amplifier configuration (left) and equations (right). ....	250
Figure 7-20. Calculating $V_{out}$ example for a differential amplifier.....	251
Figure 7-21. Inverting summing amplifier configuration (left) and equations (right). ....	251
Figure 7-22. Calculating $V_{out}$ example for an inverting summing amplifier.....	252
Figure 7-23. Non-inverting summing amplifier configuration (left) and equations (right). ....	252
Figure 7-24. Calculating $V_{out}$ example for a non-inverting summing amplifier.....	253
Figure 7-25. This non-inverting summing amplifier shifts and gains the signal, $V_{in}$ .....	253
Figure 7-26. Voltage at the non-inverting input, $V_{in(+)}$ . ....	255

Figure 7-27. Shifted and gained pH electrode voltage signal. $V_b$ shifts the signal positive, and after amplifying, the total shift is +1.65V. ....	256
Figure 7-28. Solved non-inverting summing amplifier for pH meter....	257
Figure 7-29. The bias voltage is generated using a voltage divider, and then buffered before adding it to the (buffered) probe voltage. ....	259
Figure 7-30. How do you supply negative volts? .....	260
Figure 7-31. Splitting a power supply (top) and using a voltage divider (bottom) for supplying a negative voltage to the bottom rail of an op-amp. ....	261
Figure 7-32. ICL7760 wired as a negative voltage generator (-5V out on pin 5). ....	261
Figure 7-33. Differentiator (left) and integrator (right) op-amp configurations. ....	262
Figure 7-34. Attenuating a probe signal using a voltage divider, then buffering the output.....	263
Figure 7-35. Structure of a Wheatstone bridge.....	263
Figure 7-36. Circuit diagram for Activity 7-1 (load cell scale). ....	265
Figure 7-37. Experimental setup for Activity 7-1 (load cell scale).....	266
Figure 7-38. Circuit diagram for Activity 7-2 (pH meter). ....	269
Figure 7-39. Station setup for Activity 7-1.....	272
Figure 7-40. Station setup for Activity 7-2.....	273
Figure 8-1. The effect of a carefully designed low-pass filter (LPF).....	275
Figure 8-2. Bode Magnitude Plot for a first-order LPF. ....	277
Figure 8-3. Calculation of the gain of an LPF, one decade higher than the cutoff frequency. ....	278
Figure 8-4. Worked example for an LPF, $f_c=200$ Hz. Left: passive LPF, right: active LPF with unity gain. ....	279
Figure 8-5. The effect of a carefully designed high-pass filter (HPF). ....	280
Figure 8-6. Bode Magnitude Plot for a first-order HPF.....	281
Figure 8-7. Inverting AC amplifier. Capacitor $C_1$ filters out frequencies two decades below $f_c$ . If $V^+=+5$ V, the output signal will be gained by $R_F/R_1$ , and oscillate about +2.5V.....	282
Figure 8-8. Inverting amplifier example: electret microphone preamplifier.....	282
Figure 8-9. A coupling capacitor transmits AC and blocks DC. ....	283
Figure 8-10. An example band-pass filter (top) and corresponding Bode Magnitude Plot (bottom). ....	285
Figure 8-11. Twin-T Notch Filter (left) and Bode Magnitude Plot (right). (Carter 2006, 19-26) .....	286
Figure 8-12. Passive second-order HPF. ....	286
Figure 8-13. Non-inverting, amplifying second-order LPF. ....	287

Figure 8-14. Properties of an ideal op-amp. ....	287
Figure 8-15. Balancing the inputs of an inverting op-amp with a compensating resistor.....	288
Figure 8-16. Matching the output impedance of an op-amp with the input impedance of the next stage (in this case, the MCU's analog pin). ...	289
Figure 8-17. The 16 MHz crystal oscillator on the Arduino Uno, responsible for microprocessor speed. ....	300
Figure 8-18. RTC module for keeping track of epoch time.....	301
Figure 8-19. Circuit diagram (left) of a logic shifter (photo right), safely bridging a 3.3V microSD card module to the hotter 5V logic-level MCU. ....	306
Figure 8-20. Section 8 station setup. ....	312
Figure 9-1. Piezoelectric elements.....	323
Figure 9-2. Piezoelectric buzzer plugged directly into the Arduino Uno. ....	323
Figure 9-3. Photoresistors of various sizes (5 to 12 mm). ....	325
Figure 9-4. Voltage divider for a photoresistor. ....	326
Figure 9-5. A transimpedance amplifier (left) converts current, $I_{in}$ to voltage, $V_{out}$ with a gain of $R_F$ . An example (right) shows the LM358 amplifying the current through an LDR, with a bias voltage $V_b$ to raise the signal into the output voltage swing of the amp ( $\sim 0.1 \text{ V} - 3.9\text{V}$ for op-amp supplies $V^+ = +5\text{V}$ and $V^- = \text{GND}$ ). ....	327
Figure 9-6. The PD638C photodiode.....	328
Figure 9-7. A photodiode wired in the voltage divider configuration with sense resistor (left), and as an input for a transimpedance amplifier (right). ....	328
Figure 9-8. The PT334-6C phototransistor (right), wrapped in electrical tape (left). ....	329
Figure 9-9. A phototransistor wired in the voltage divider configuration with sense resistor (left), and as an input for a transimpedance amplifier (right). ....	329
Figure 9-10. TSL235R light-to-frequency converter. ....	330
Figure 9-11. Toshiba TCD1304AP linear CCD. ....	332
Figure 9-12. BH1750 Light Sensor module.....	333
Figure 9-13. Low-cost laser light receiver. ....	334
Figure 9-14. TCS3200 colour detection module. ....	334
Figure 9-15. A comparator op-amp with a carefully-selected bias voltage changes a small signal response into a digital signal (HIGH or LOW). ....	338
Figure 9-16. Mapping the pins of a matrix keypad to rows and columns. ....	338

Figure 9-17. A custom LED matrix display. ....	340
Figure 9-18. A SN74HC595 shift-out register, with digital output pins Q0 – Q7. ....	343
Figure 9-19. A SN74HC165 shift-in register, wired to send the pin states from digital input pins Q0 – Q7. In this configuration, pin 15 has been wired to ground, so the chip is constantly enabled, requiring one less control wire from the MCU. ....	346
Figure 9-20 Configuring the ATmega328 chip outside the Arduino Uno. Pin numbers follow the physical layout of the DIP chip (Pin 1 is RESET). ....	349
Figure 9-21. USBtinyISP chip programmer, useful for re-burning the bootloader onto an MCU, uploading a sketch through the ICSP header on the Arduino Uno, or programming an MCU directly through the appropriate pins. ....	350
Figure 10-1. Using port registers to set and read digital pin 12 (PB4), in Bank B. ....	367
Figure 10-2. Momentary switch connected to INT0 (digital pin 2). ....	369
Figure A-1. Troubleshooting flowchart: developing resilience. ....	409
Figure A-2. Potential areas to consider troubleshooting. Many problems are multifaceted, involving more than one area. ....	409
Figure A-3. A 50% duty cycle square wave generator configuration for the 555 timer (LMC555 CMOS version required above ~400 kHz). Ranges for $f_{out}$ were obtained experimentally using a LMC555 timer and monolithic capacitors. ....	421
Figure A-4. Voltage divider network at an op-amp input: solving for the input voltage. ....	433
Figure A-5. Pin-out diagram for a generic Arduino Uno r3. Pin numbers (2 to 28) correspond to the pin numbers on the ATmega328 chip. (Atmel Corporation 2016). ....	436
Figure A-6. Pin-out diagram for the ATmega328 28-pin (DIP). Pin labels for the Arduino IDE are indicated in blue (~ indicates PWM-capable). (Atmel Corporation 2016). ....	437
Figure A-7. Pin-out diagram for the ATTiny85 8-pin (DIP version). Pin labels for the Arduino IDE are indicated in blue (~ indicates PWM-capable). (Atmel Corporation 2013). ....	437
Figure A-8. List of circuit diagram symbols used in this text. Note that many variants of these symbols are common. LDRs, LEDs, photodiodes, transistors, and MOSFETs often appear in circuit diagrams without circles. ....	438

Figure A-9. Summary conversion chart for common variable types. Grey  
lines: *casting* (see Table 3-5). Black lines: see Table 3-6 for examples.  
See Table 10-23 for advanced formatting with Strings..... 439

## LIST OF TABLES

Table 1-1. Typical voltages and current capacities for various battery types and chemistries. (Wenzel 2017) .....	16
Table 1-2. Current capacity for common wire gauges. (Scherz and Monk 2016).....	17
Table 1-3. Summary chart: resistors in series vs. resistors in parallel. ....	32
Table 1-4. Measured and calculated values for Activity 1-1. ....	40
Table 1-5. Measured and calculated values for Activity 1-2. ....	41
Table 2-1. Recommended operating conditions for the LM317 voltage regulator (TO-220 package). (Texas Instruments Inc 2016a) .....	54
Table 2-2. Some electrical characteristics of the NE555 chip. (Texas Instruments Inc 2014b) .....	68
Table 2-3. Logic tables for a 2-input AND gate. “0V” is the same as “ground”, and this table assumes that <i>logic level</i> for your circuit is +5V. ....	71
Table 2-4. Two-input AND logic table.....	71
Table 2-5. Two-input OR logic table.....	73
Table 2-6. NOT logic table.....	74
Table 2-7. Two-input NAND logic table.....	74
Table 2-8. Two-input NOR logic table.....	75
Table 2-9. Two-input XOR logic table.....	75
Table 2-10. Two-input XNOR logic table.....	76
Table 2-11. Logic table for Example 1(a).....	77
Table 2-12. Logic table for Example 2(a).....	77
Table 2-13. Experimental results from Activity 2-1.....	79
Table 3-1. Bit depth size chart.....	92
Table 3-2. Mathematical operators and functions in C++.....	94
Table 3-3. Relational operators in C++ .....	100
Table 3-4. Table of logical (Boolean) operators.....	102
Table 3-5. How to cast between common variable types, with examples .....	106
Table 3-6. More complicated variable conversions involving String and char .....	110
Table 3-7. C++ shorthand.....	112
Table 3-8. Three major types of loops performing the same task.....	115
Table 4-1. Wiring a momentary switch to a digital input pin .....	129